
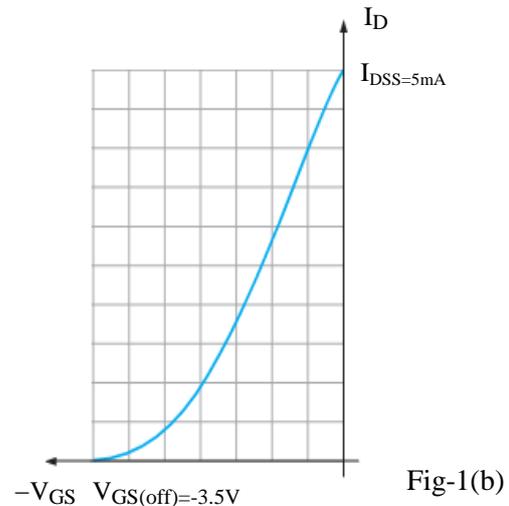


Department of Higher Education
University of Computer Studies, Yangon
Third Year (B.C.Tech.)
Final Examination
Electronics I (CT 304)
September, 2018


Answer all questions.

Time allowed: 3 hours

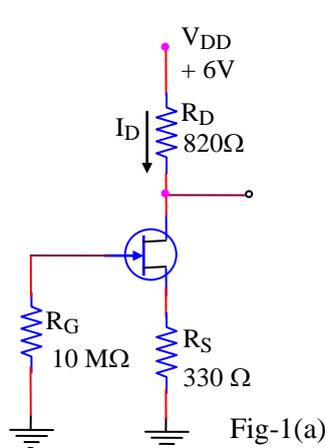- 1(a) Find V_{DS} and V_{GS} in Fig 1(a). When $I_D = 8 \text{ mA}$. (10 marks)
 (b) Graphically determine the Q-point for the circuit in Fig1(a) using the transfer characteristic curve in Figure 1(b). (10 marks)



- 2(a) For the unloaded amplifier in Fig 2(a), find V_{GS} , I_D , V_{DS} and the rms output voltage V_{ds} .
 $I_{D(on)} = 8 \text{ mA}$ at $V_{GS} = 12 \text{ V}$, $V_{GS(th)} = 4\text{V}$ and $g_m = 4500\mu\text{S}$. (10 marks)
 (b) From datasheet $I_{DSS} = 3\text{mA}$, $V_{GS(off)} = -6\text{V}$ maximum and $g_{m0} = 5000\mu\text{S}$. Using these value, determine the forward transconductance for $V_{GS} = -4\text{V}$ and find I_D at this point. (10 marks)

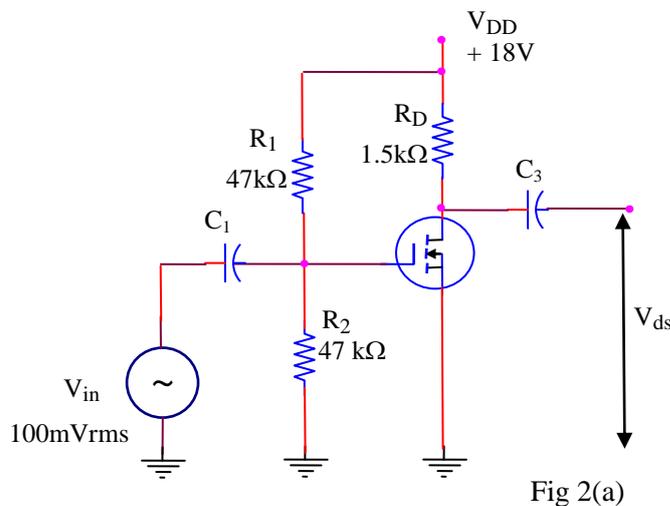

3(a) If a signal voltage of 10mVrms is applied to each amplifier in Fig-3(a), what are the output voltages and what is their phase relationship with inputs? (10 marks)

(b) Determine A_{ol} for the following values of f . Assume $f_{c(ol)}=200$ Hz and $A_{ol(mid)}=80000$.

- (i) $f=2$ Hz (ii) $f=10$ Hz (iii) $f=100$ Hz (iv) $f=2500$ Hz

(10 marks)

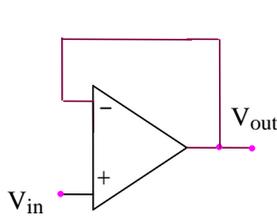


Fig 3(a-i)

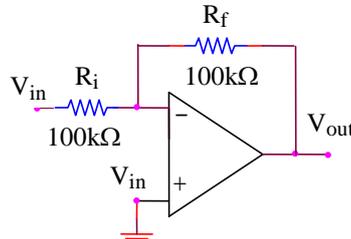


Fig 3(a-ii)

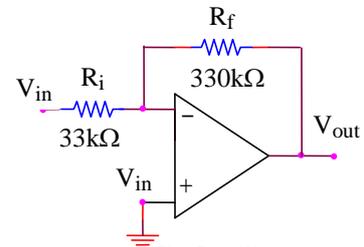


Fig 3(a-iii)

4(a) Determine the weight of each input voltage for the scaling adder in Fig4 (a) and find the output voltage. (10 marks)

(b) Determine the output voltage of the op-amp differentiator in Fig. 4(b) for the triangular-wave input shown. (10 marks)

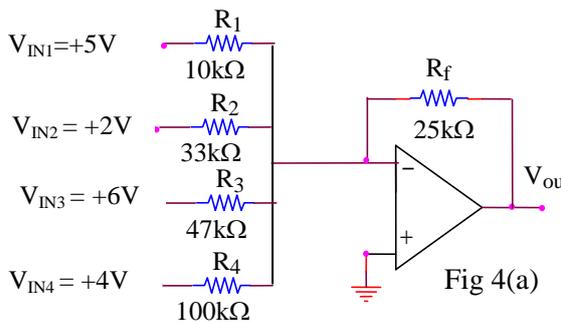


Fig 4(a)


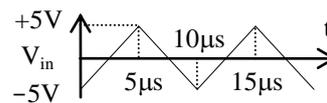


Fig. 4(b)

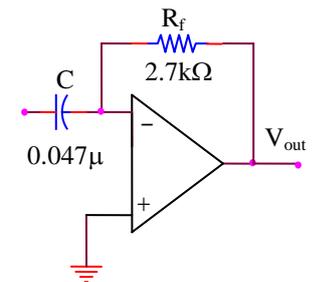

5(a) Determine the critical frequency of the Sallen-Key high-pass filter in Fig 5(a), and set the value of R_1 for an approximate Butterworth response. (DF=1.414) (10 marks)

(b) Determine the center frequency, maximum gain, and bandwidth for the filter in Fig. 5(b). (10 marks)

(10 marks)

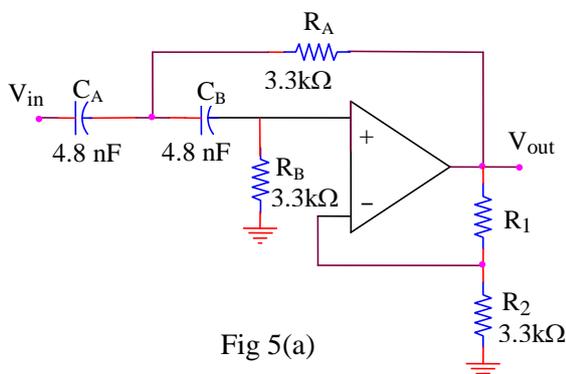


Fig 5(a)

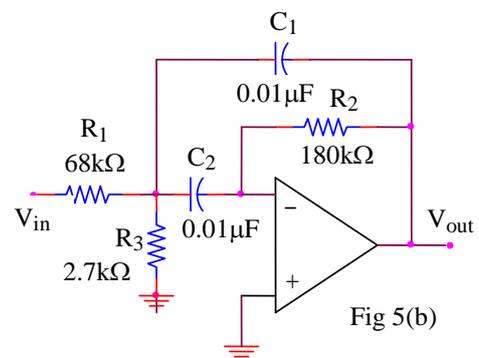


Fig 5(b)
